

## (4) Circuit Theorems


### Superposition Theorem:

\* ଧାରଣା: ଧାରଣା (current/voltage source) ଧାରଣା ଧାରଣା source solve କରା ଧାରଣା ଧାରଣା ଧାରଣା ଧାରଣା ଧାରଣା (ଧାରଣା ଧାରଣା original circuit

କାହିଁ source ଧାରଣା?


Voltage source off  $\rightarrow$  using short circuit  
current " "  $\rightarrow$  " open "

### Ex-4.3

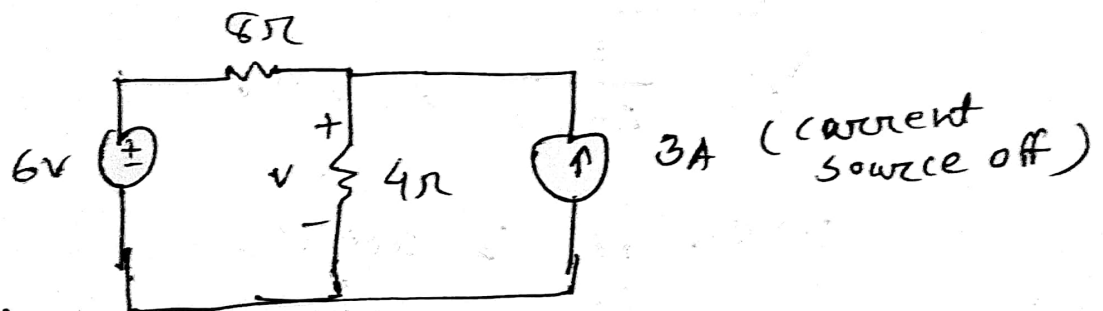

Find  $v$  using superposition theorem


Ans: When 6V is active,

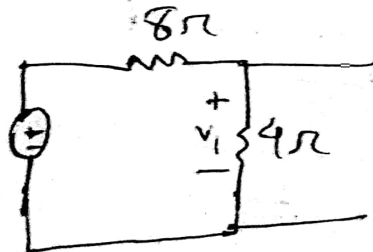

[series]  
voltage divider rule

$$v_1 = \frac{4}{8+4} \times 6 = 2V$$

When 3A is active,

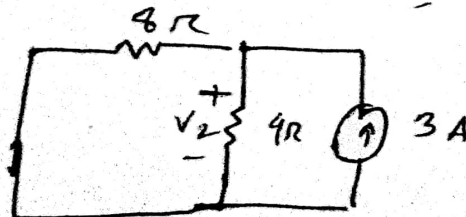

[Parallel]  
current divider rule


$$i_2 = \frac{2/4}{2/4 + 2/8} \times 3 = 2A$$

$$v_2 = i_2 \times 4 = 2 \times 4 = 8V$$

[current resistance]

$$\therefore V = v_1 + v_2 = 2 + 8 = 10V$$

# Practice Problem 9.3

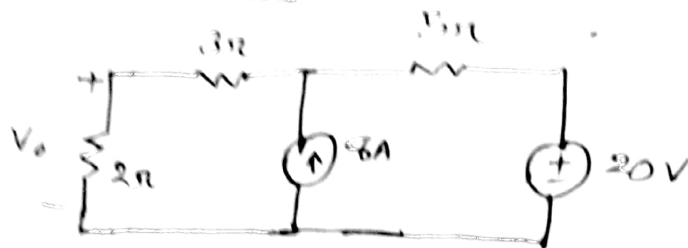


Voltage / same  
5Ω + 11Ω + 2Ω

Find  $V_o$


Ans:

When 20V is active,

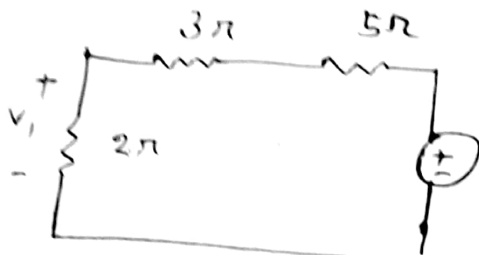

$$V_1 = \frac{2}{2+3+5} \times 20 = 4V$$

When 8A is active,

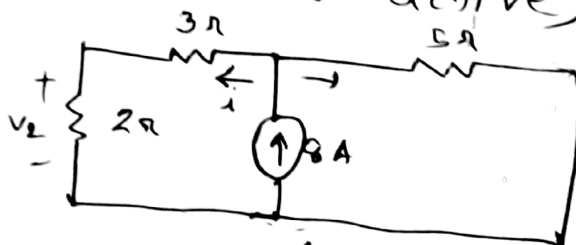


$$i = \frac{1}{\frac{1}{2+3} + \frac{2}{5}} \times 8 = 4A$$

$$V_2 = iR = 4 \times 2 = 8V$$

$$V_o = V_1 + V_2 = 4 + 8 = 12V \leftarrow \text{Superposition theorem}$$


Practice Problem - 9.9 (modified)

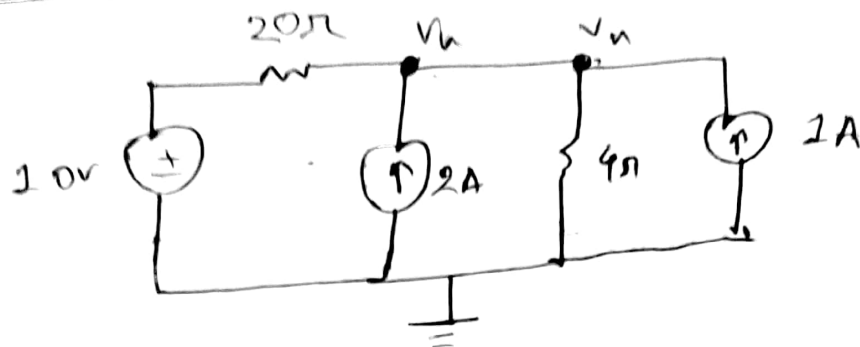

Find  $V_u$


$V_u \rightarrow$  ending point ground -  $\downarrow$

Ans: When 10V is active

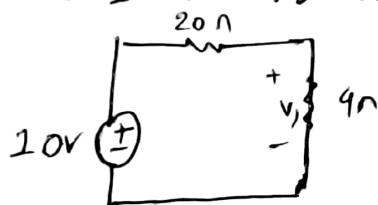

$$\therefore V_1 = \frac{4}{20+4} \times 10 = 1.67V$$


When 2A is active,

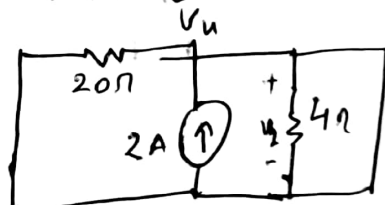

$$I_1 = \frac{1}{\frac{1}{\frac{20}{20}} + \frac{1}{4}} \times 2 = 1.67A$$

$$V_2 = I_1 R = 1.67 \times 4 = 6.68V$$

When 1A is active,

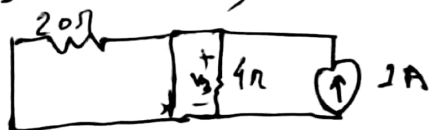

$$I_2 = \frac{1}{\frac{1}{4} + \frac{2}{20}} \times 1 = 0.833A$$


$$V_3 = I_2 R = 0.833 \times 4 = 3.332$$

$$V_u = V_1 + V_2 + V_3 = 1.67 + 6.68 + 3.332 = 11.682V$$

Ans.


(9) Please (Circuit Theorems)  
(2nd Part)

Ex - 9.6

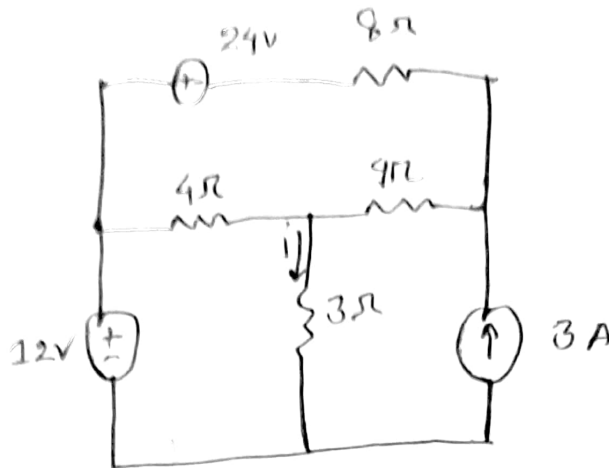

Find  $i$  using superposition theorem

Ans. When 12V is active,

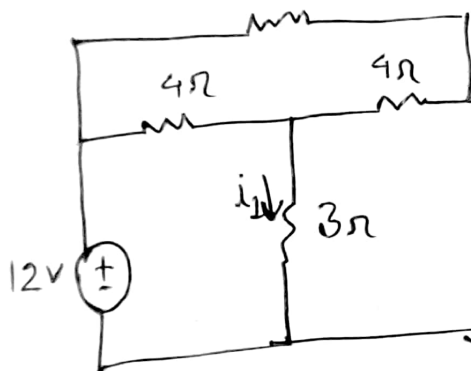


← short circuit for V

(एक पावर 8Ω को एक पावर 4Ω में)

← open circuit for A

→ No need this wire

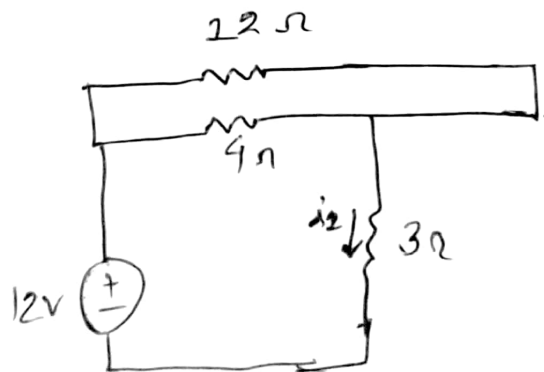
$8 + 4 = \text{series,}$   
 $12 \parallel 4,$



← एक पावर 8Ω को एक पावर 4Ω में  
एक 2A (4A) पावर

$$i_1 = \frac{V}{R} = \frac{12}{6} = 2A \quad [\text{Ohm's Law}]$$

When 3A is active

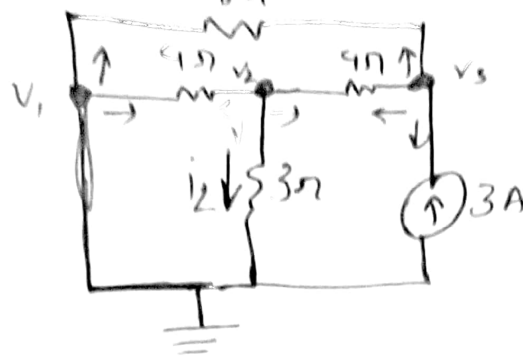

$V_1 = 0V$  [source] source (not)

Node 2:

$$\frac{V_2 - 0}{4} + \frac{V_2 - 0}{3} + \frac{V_2 - V_3}{4} = 0$$

$$(1/4 + 1/3 + 1/4)V_2 - 1/4 V_3 = 0 \quad \text{--- (i)}$$



Node 3:

$$\frac{V_3 - V_2}{4} - 3 + \frac{V_3 - V_1(0)}{6} = 0$$

$$-1/4 V_2 + (1/4 + 1/6)V_3 = 3 \quad \text{--- (ii)}$$

$$V_2 = 3V \quad V_3 = 10V$$

$$i_2 = \frac{V}{R} = \frac{3}{3} = 1A$$

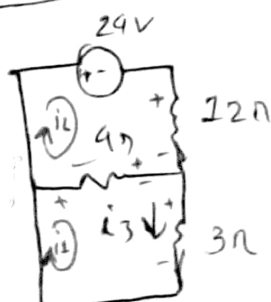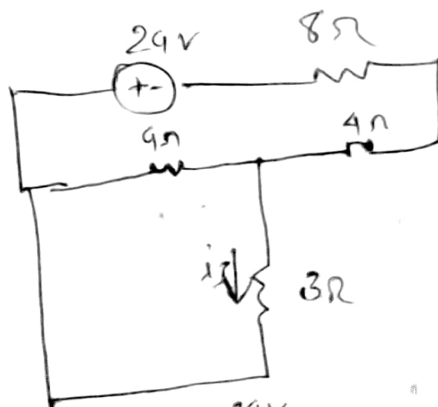

$$6 + 4 = 12 \Omega$$

Mesh-1:  $-4(i_1 - i_2) - 3i_1 = 0$   
 $-7i_1 + 4i_2 = 0 \quad \text{--- (i)}$

Mesh-2:

$$-24 - 12i_2 - 4(i_2 - i_1) = 0$$

$$4i_1 - 16i_2 = 24 \quad \text{--- (ii)}$$

$$i_1 = -1A$$

$$i_2 = -1.75$$


$$i_3 = i_2 = -1A$$

$$i = i_1 + i_2 + i_3$$


$$= 2 + 1 + (-1) = 2A$$

### Thevenin's Theorem

Simplest circuit, 1 source, 1 resistance

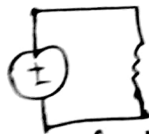


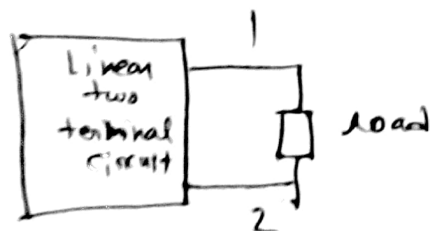complicated circuit  $\rightarrow$  simplest circuit  $\rightarrow$  Thevenin's circuit



$R_{th} = \text{Thevenin}$


Ex - 4.8

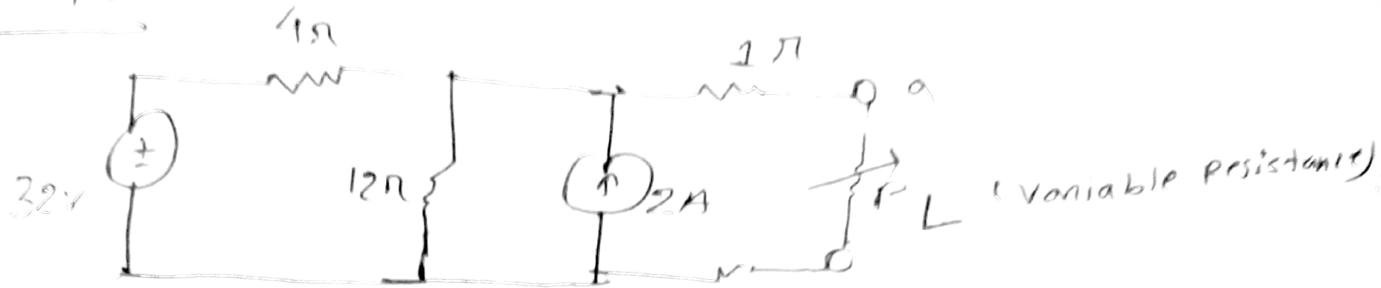


Find the Thevenins equivalent circuit

Ans:

Step 1: Open the load terminal

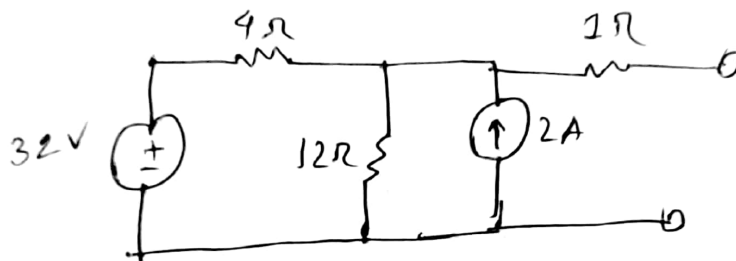


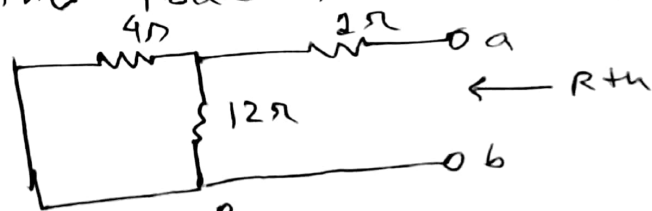Step 2: Turn off all sources & calculate  $R_{th}$  from the load terminal.



$$R_{th} = 1 + (4 \parallel 12) = 4\Omega$$

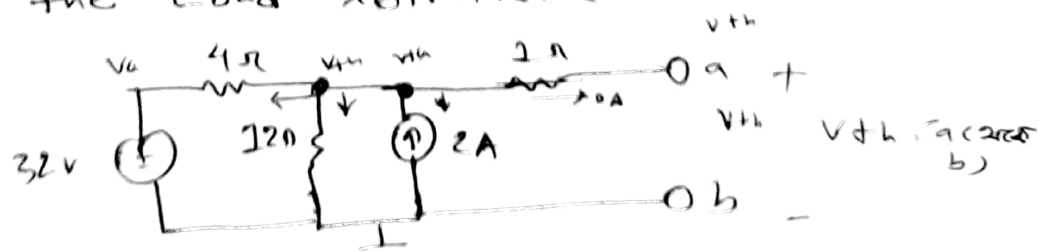Step 3: Return all sources and find  $V_{th}$  from the load terminal.



best apply mesh analysis

$$V_1 = 0 \times 1\Omega = 0V \text{ (acting like a short circuit)}$$

$$\left. \begin{aligned} V_a &= 32V \\ \frac{V_{th} - 32}{4} + \frac{V_{th}}{12} - 2 &= 0 \end{aligned} \right\} \begin{aligned} (2/4 + 1/12)V_{th} &= 2 \\ V_{th} &= 30V \end{aligned}$$


Step 4: Draw the Thevenin equivalent circuit using  $V_{th}$ ,  $R_{th}$ , and load.



Ans.

$$R_{th} = 4\Omega$$

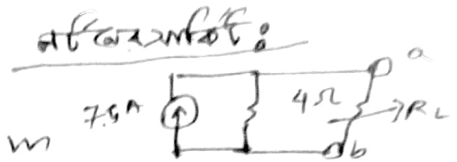
$$I_N = \frac{V_{th}}{R_{th}} = \frac{30}{4} = 7.5A \text{ Norton's Theorem}$$



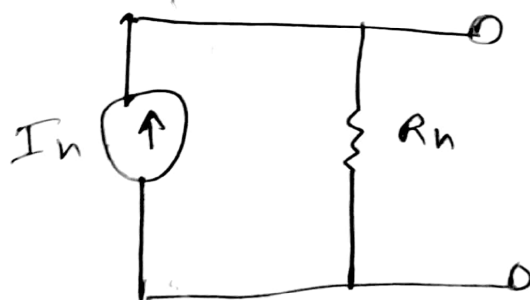(2) A complicated circuit can be converted into a current source and a parallel resistance circuit.

Thevenin  $\rightarrow$  voltage source, current & series Resistance

Norton  $\rightarrow$  current source, current & parallel Resistance



$$R_n = R_{th}$$

$$I_n = \frac{V_{th}}{R_{th}}$$



Maximum Power Transfer Theorem:  $R_L$  is variable


resistance) only  $R_L$  is max power  
 (Source is constant, max power  
 transfer occurs when  $R_L = R_{th}$ )

Source is constant load -  $\rightarrow$  maximum power transfer

when  $R_L = R_{th}$


Q: Find the value of  $R_L$  for which maximum power transfer occurs?

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

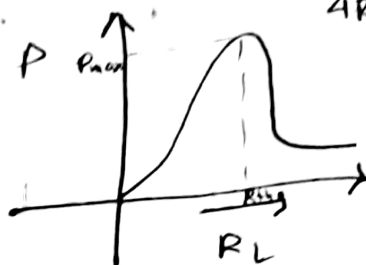


$$R_L = 4\Omega, P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{30^2}{4 \times 4} = \frac{56.25}{1} = 56.25 \text{ W}$$

### Practice Problem 4.8

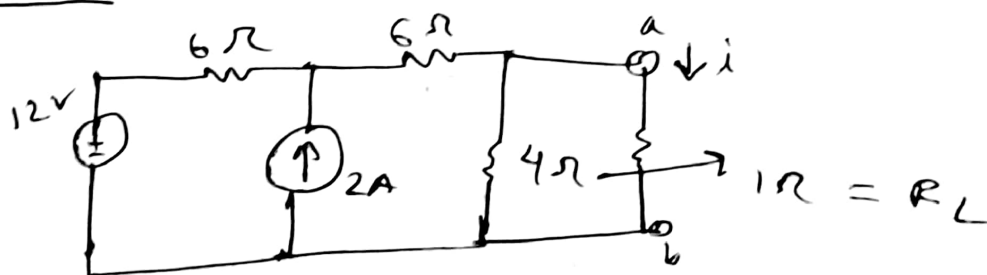


- Find Thevenin's Equivalent Circuit.
- " Norton's "
- " the value of  $R_L$  for maximum power transfer
- Find the value of maximum power
- Find the value of  $i$  for  $R_L = 1\Omega$

a)

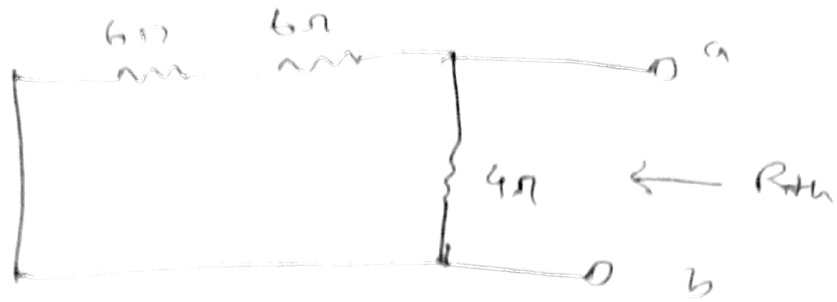

$$R_{th} = (6+6) \parallel 4 = 3\Omega$$

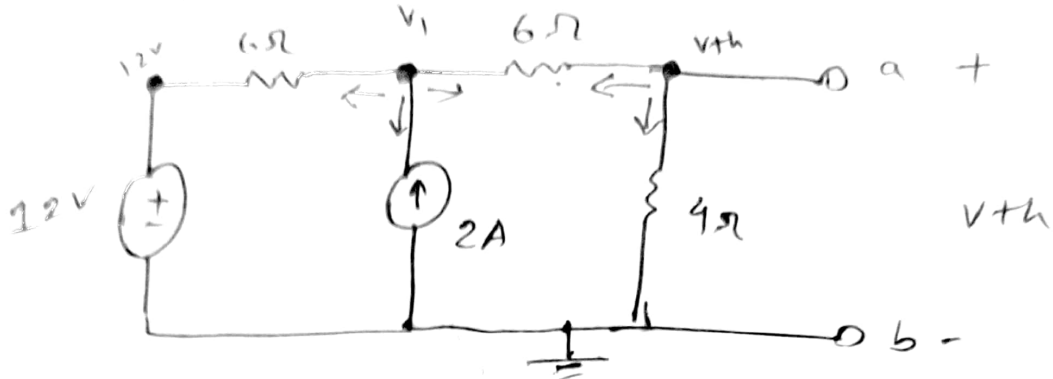

[ Node (a) voltage  $v_{th}$  and 2A current source (b) current ]

$v_1$  is at node,

$$\frac{v_1 - 12}{6} + \frac{v_1 - v_{th}}{6} - 2 = 0$$

$$\left(-\frac{2}{6} + \frac{2}{6}\right)v_1 - \frac{2}{6}v_{th} = 4 \quad \text{--- (i)}$$

$v_{th}$  is at node,

$$\frac{v_{th} - v_1}{6} + \frac{v_{th}}{4} = 0$$

$$-2/6 v_1 + (2/6 + 2/4) v_{th} = 0 \quad \text{--- (ii)}$$

$$v_1 = 15V$$


$$v_{th} = 6V$$

Thevenin's Equivalent circuit,



$$b) R_N = R_{th} = 3\Omega$$
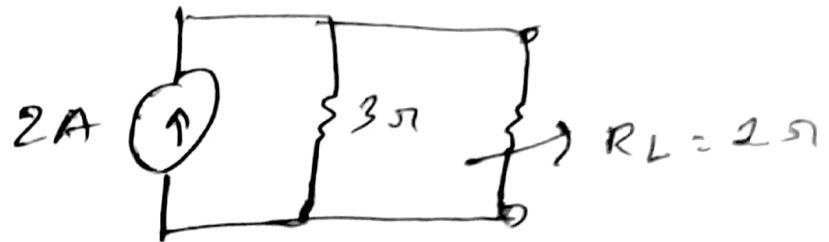
$$I_N = \frac{V_{th}}{R_{th}} = \frac{6}{3} = 2A$$



$$c) R_L = R_{th} = 3\Omega$$

$$d) P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{6^2}{4 \times 3} = \frac{36}{12} = 3W$$

e) From Thevenin's Equivalent Circuit,

$$\text{ohm's law, } i = \frac{V}{R_{eq}} = \frac{6}{3+2} = \frac{6}{5} = 1.2A$$