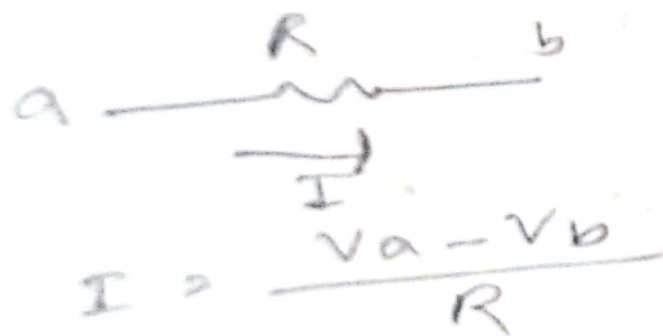



(3) Methods of Analysis

- i) Nodal Analysis, — current eq.
- ii) Mesh Analysis — voltage eq.



A circuit diagram showing a resistor labeled 'R' connected between two nodes, 'a' and 'b'. Node 'a' is on the left and node 'b' is on the right. A current 'I' is indicated by an arrow pointing from node 'a' to node 'b' through the resistor.


$$I = \frac{V_a - V_b}{R}$$

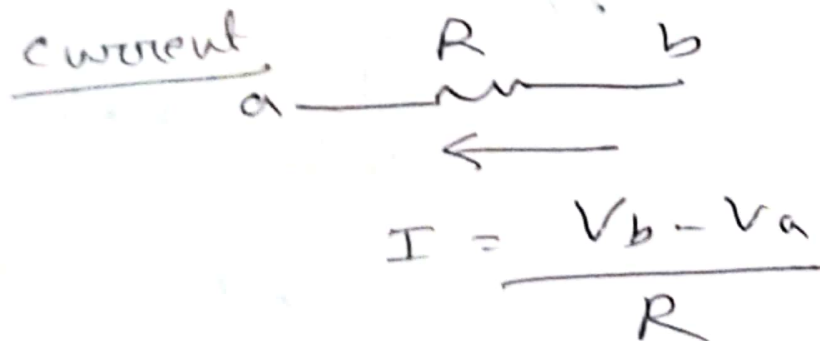

A circuit diagram showing a resistor labeled 'R' connected between two nodes, 'a' and 'b'. Node 'a' is on the left and node 'b' is on the right. A current 'I' is indicated by an arrow pointing from node 'b' to node 'a' through the resistor. The word 'current' is written above the resistor.

$$I = \frac{V_b - V_a}{R}$$

$$V_{ab} = V_a - V_b$$

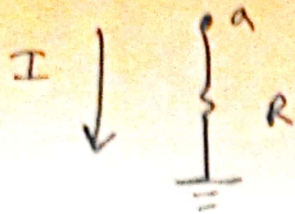


$$I = \frac{V_a - V_g}{R}$$

$$= \frac{V_a - 0}{R}$$

$$= \frac{V_a}{R}$$

voltage
resistance

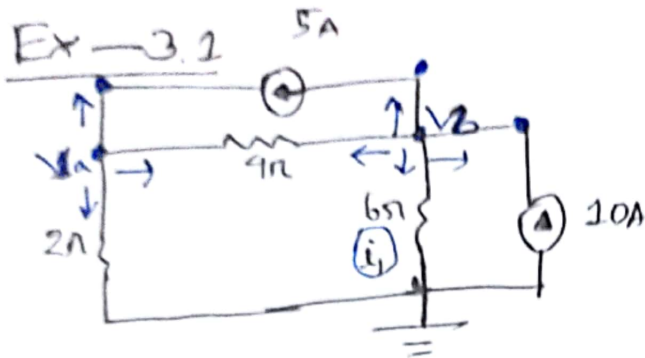

$$i_1 = \frac{V_b - 0}{6} = \frac{20}{6} = 3.33A$$

$$i_2 = \frac{V_a - V_b}{4} \text{ Direction opposite}$$

Calculate the Node Voltages

Ans: 2 Node equation [Ground arch]

Node A : ↓ 5A 5A5 $\frac{V_a - 0}{R} = \frac{V_a}{2}$

$\frac{V_a}{2\Omega} + \frac{V_a - V_b}{4\Omega} - 5 = 0$ [↑ 5A 5A5 Direction ←]

$$\Rightarrow \left(\frac{1}{2} + \frac{1}{4}\right) V_a - \frac{1}{4} V_b = 5 \quad \text{--- (i)}$$

Node B : $\frac{V_b}{6} + \frac{V_b - V_a}{4} + 5 - 10$

$$\Rightarrow -\frac{2}{4} V_a + \left(\frac{1}{6} + \frac{2}{4}\right) V_b = 5 \quad \text{--- (ii)}$$

By solving (i) & (ii) we get, $V_a = 13.33V$


$$V_b = 20V$$

$$[a_1x + b_1y = c_1]$$

Power dissipation in 6Ω

$$P_{6\Omega} = i_1^2 \times 6 = 3.33^2 \times 6$$

Practice - 2

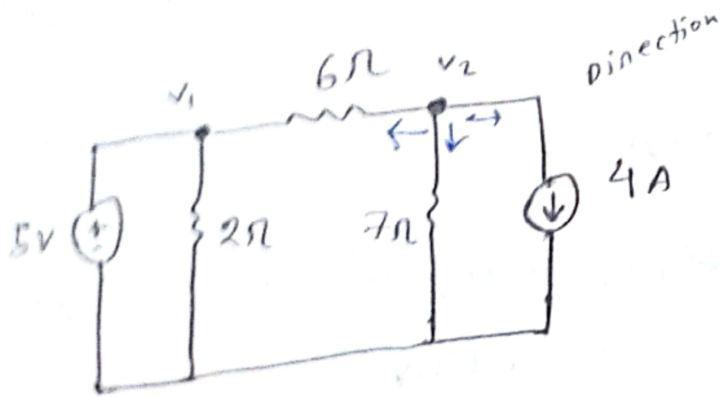

$V_1 = 5V$, $\text{KVL} \Rightarrow V_1 = -5V$

corresponding voltage source KVL equation across 2Ω resistor,


Note - 2

$$\frac{V_2 - V_1(5V)}{6} + \frac{V_2}{7} + 4 = 0$$

$$\Rightarrow \left(\frac{2}{6} + \frac{2}{7}\right)V_2 = -4 + \frac{5}{6}$$

$$\therefore V_2 = -3.16V$$

Practice - 2

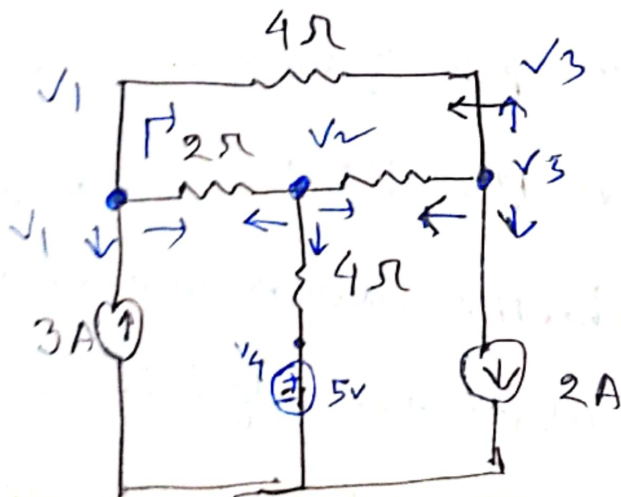

Ground - Reference Node

V - Non " "

$V_2 \text{ --- } \oplus \text{ --- } V_3$
super node X

Find the node voltages

Ans

$$\begin{aligned} \text{Node-1} \\ \frac{-3}{(\downarrow)} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} (\leftarrow) = 0 \\ \Rightarrow \left(\frac{1}{2} + \frac{1}{4} \right) V_1 - \frac{1}{2} V_2 - \frac{1}{4} V_3 = 3 \quad \text{--- (i)} \end{aligned}$$

$$\begin{aligned} \text{Node-2} \\ \frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_2 - V_3}{8} = 0 \\ \Rightarrow -\frac{1}{2} V_1 + \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) V_2 - \frac{1}{8} V_3 = 0 \quad \text{--- (ii)} \end{aligned}$$

$$\begin{aligned} \text{Node-3} \\ \frac{V_3 - V_2}{8} + 2 + \frac{V_3 - V_1}{4} = 0 \\ \Rightarrow -\frac{1}{4} V_1 - \frac{1}{8} V_2 + \left(\frac{1}{4} + \frac{1}{8} \right) V_3 = -2 \quad \text{--- (iii)} \end{aligned}$$

$$V_1 = 6.85V, \quad V_2 = 4V, \quad V_3 = 0.57V$$

$$i_0 = \frac{6.85 - 0.57}{4} = 1.57A$$

$$i_1 = \frac{V_2}{4} = 1A$$

$$P_{4\Omega} = 1 \times 4 = 4W$$


Mesh Analysis:

- Apply KVL - Voltage Equation

- No. of mesh - no. of equation

Ex-35

Find I_1, I_2, I_3

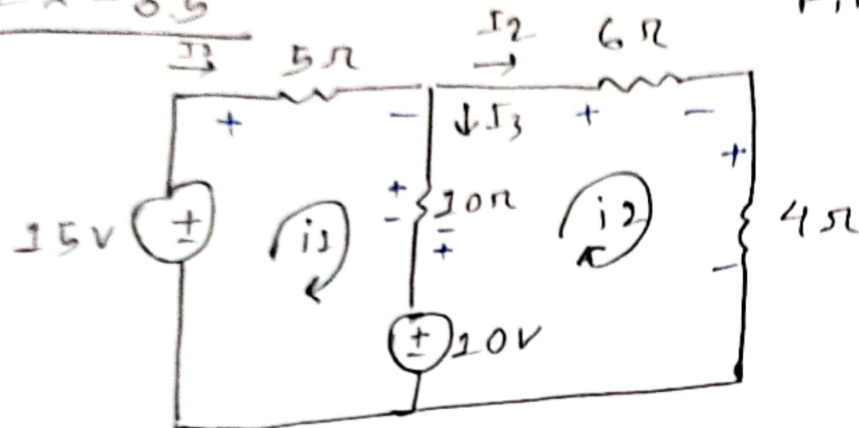

Mesh analysis में, overlapping ब्रं
आइसलेशन की- clockwise/anticlockwise चलाए गए

Mesh 1

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$\Rightarrow 3i_1 - 2i_2 = 1 \quad \text{--- (i)}$$

Mesh 2

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

$$\Rightarrow i_1 = 2i_2 - 1 \quad \text{--- (ii)}$$

+ , -
शर्त +
बिना
रुद्धि

$$i_1 = 1A, i_2 = 1A, i_3 = i_1 - i_2 = 0A$$


$$I_1 = i_1 = 1A, I_2 = i_2 = 1A$$

[i_1, i_3 चला-बिना]

[5Ω मध्य]

[6Ω मध्य]

Practice-3.5

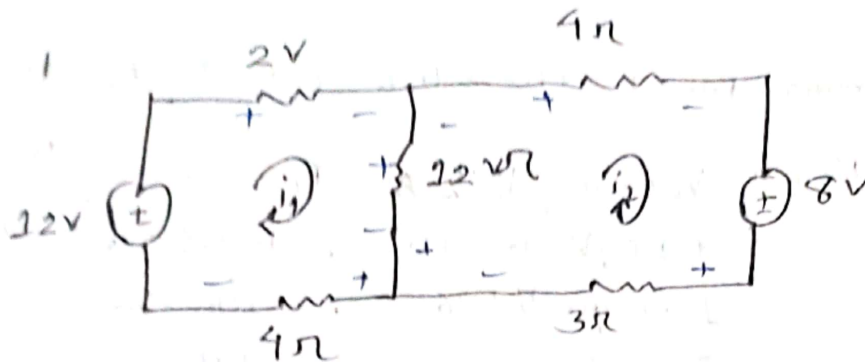

→ 2A current source
voltage source
Equation list
2A

→ 2A current source
⇒ 2A current source

Find mesh currents i_1, i_2

Ans:

Mesh-1:

$$12 - 2i_1 - 12(i_1 - i_2) - 4i_1 = 0$$

$$\Rightarrow -18i_1 + 12i_2 = -12 \quad \text{--- (i)}$$

Mesh-2:

$$-12(i_2 - i_1) - 4i_2 - 8 - 3i_2 = 0$$

$$\Rightarrow 12i_1 - 24i_2 = 8 \quad \text{--- (ii)}$$

$$i_1 = 0.67A, \quad i_2 = 0A$$


$$V_{\text{across } 2\Omega} = 2 \times i_2 = 0V$$

$$P_{2\Omega} = i_1^2 \times 2 = 0.67^2 \times 2 W$$

$$P_{12\Omega} (\text{common}) = (i_2 - i_1)^2 \times 12$$

$$(i_2 - i_1) \times 12$$

Practice - 3.6 (modified)

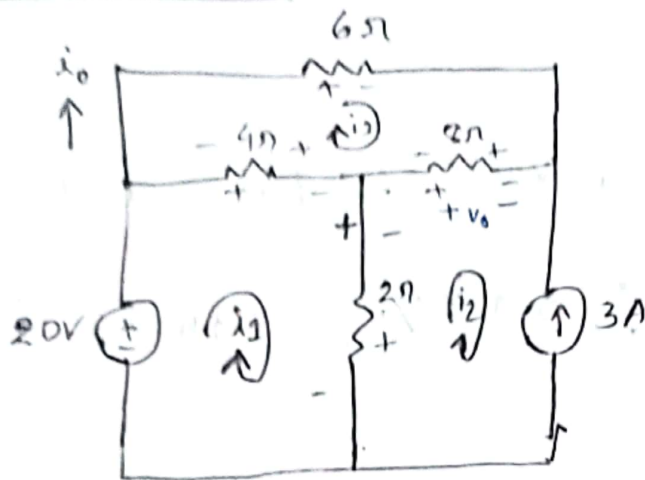

- (1) sign correct?
 (2) sign correct
 (3) Equation correct

Find mesh currents and i_o

Ans:

$$i_2 = -3A$$

Mesh - 1:

$$20 - 4(i_1 - i_3) - 2(i_1 - i_2) = 0$$

$$\Rightarrow -6i_1 + 2i_2 + 4i_3 = -20$$

$$\Rightarrow -6i_1 + 4i_3 = -20 + 6$$

$$\Rightarrow -6i_1 + 4i_3 = -14 \quad \text{--- (i)}$$

Mesh - 3:

$$-6i_3 - 6(i_3 - i_2) - 4(i_3 - i_1) = 0$$

$$\Rightarrow -6i_3 - 6i_3 - 24 - 4i_3 + 4i_1 = 0$$

$$\Rightarrow 4i_1 - 18i_3 = 24 \quad \text{--- (ii)}$$

$$i_1 = 1.70A$$

$$i_3 = -0.96A$$

$$i_2 = -3A$$

$$i_o = i_3 = -0.96A$$

Voltage across 8Ω , $V_{8\Omega} = 8 \times (i_2 - i_3)$

अतः $V_o = 8 \times (-3 - (-0.96))$

Voltage across 2Ω , $V_{2\Omega} = 2 \times (i_2 - i_1)$

$$P_{2\Omega} = (i_2 - i_1)^2 \times 2$$