
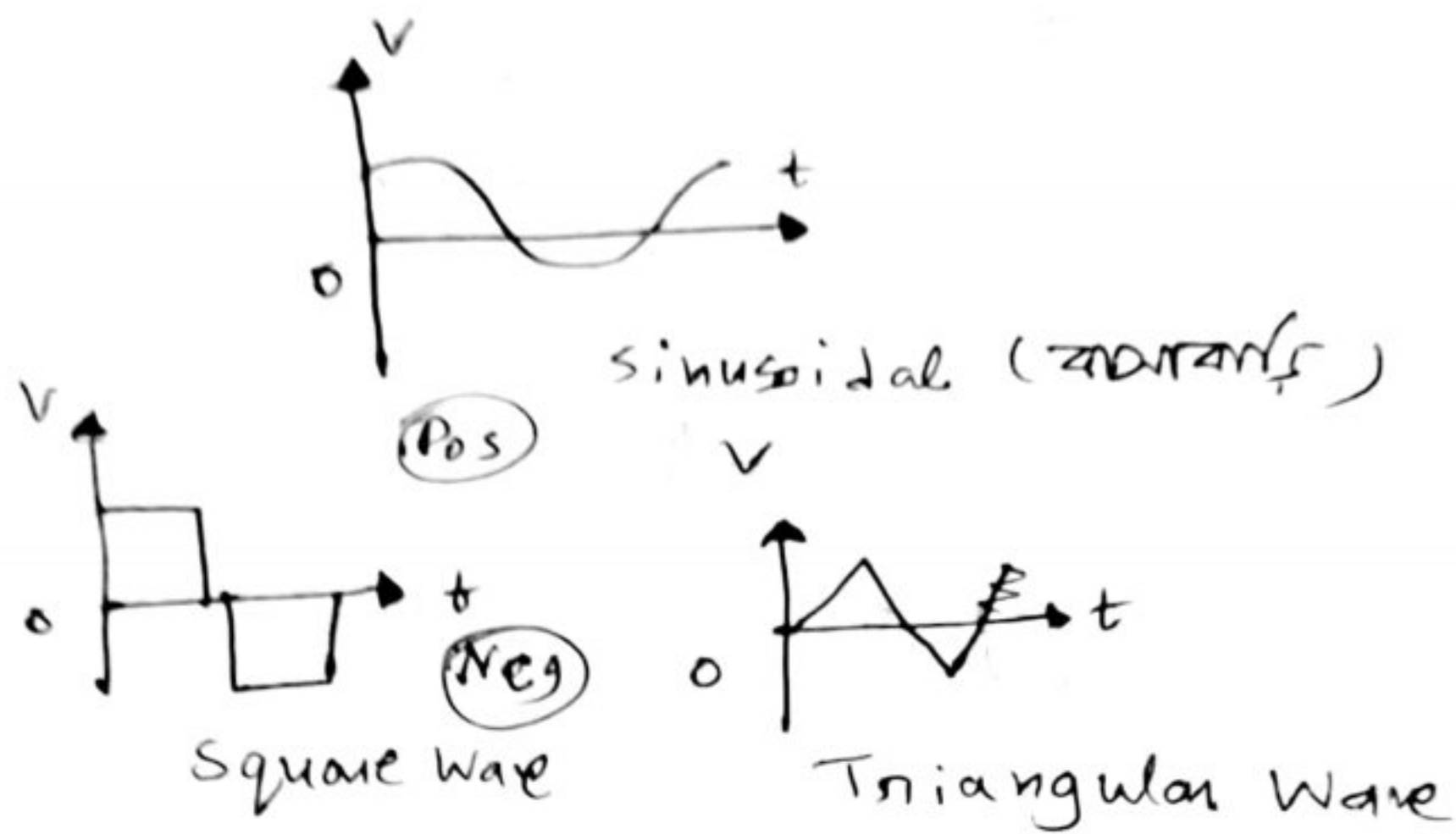


(13) Sinusoidal Alternating Waveforms

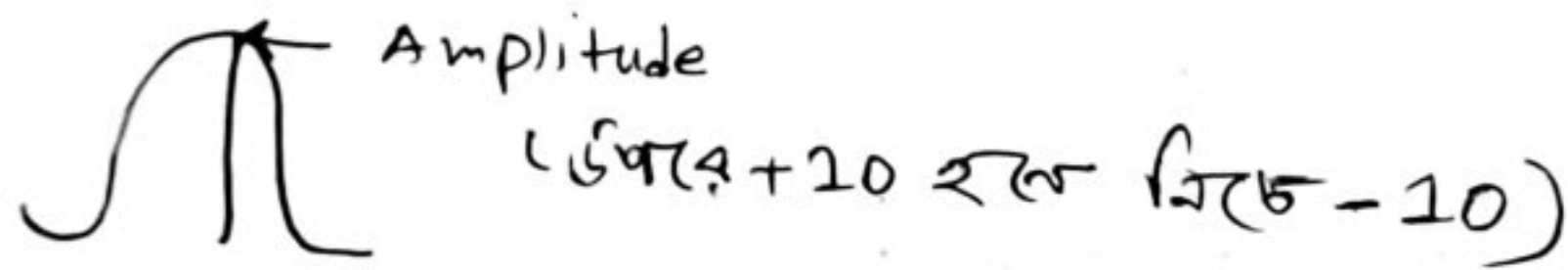

Positive & negative half-cycle.

Cycle = pos + neg (1) time period



Peak to peak = Amplitude $\times 2$


maximum = crest

minimum = trough

Time period = time taken for one complete cycle (crest to crest or trough to trough)

Frequency, $f = \frac{1}{T}$


①

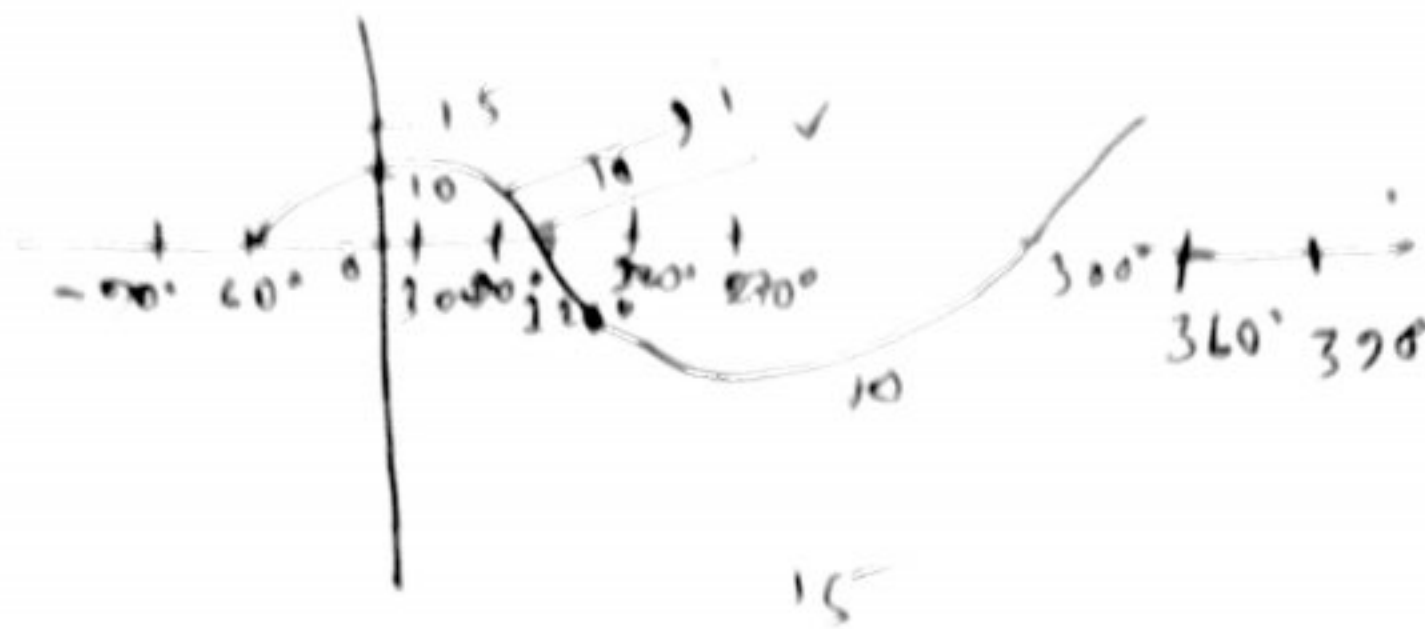

① phase difference $(-60^\circ - 30^\circ) = 90^\circ$

② i leads v by 90°

The Sine Wave

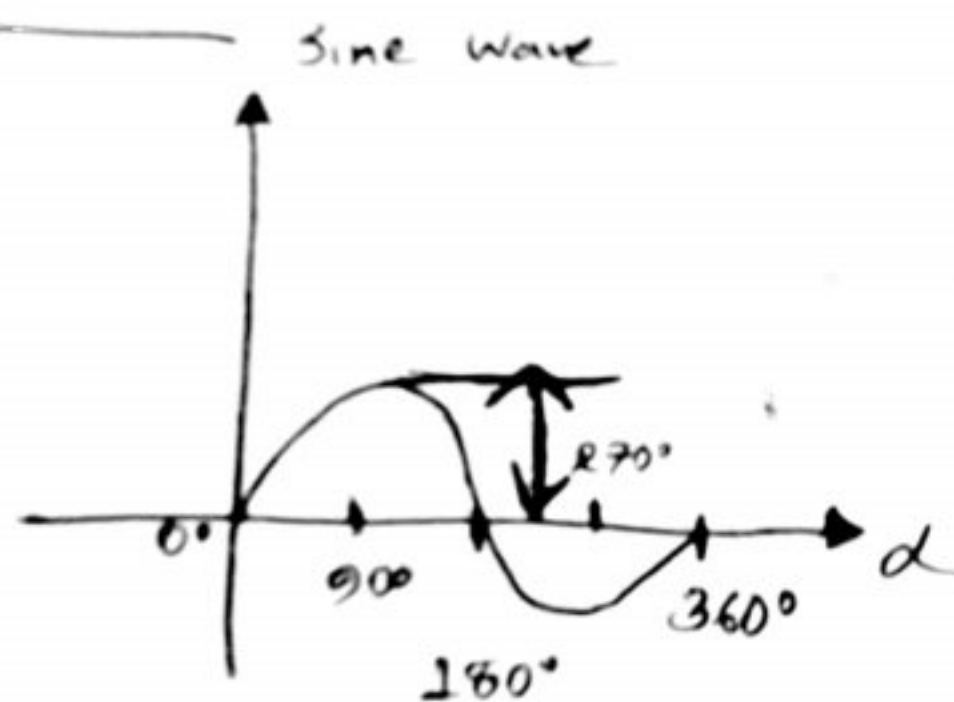

$$180^\circ = \pi$$

$$360^\circ = 2\pi$$

$$\text{Radians} = \left(\frac{\pi}{180^\circ} \right) \times (\text{degrees})$$

$$\text{Degrees} = \left(\frac{180^\circ}{\pi} \right) \times (\text{radians})$$

$$\omega = \frac{2\pi}{T} \quad \left| \quad \begin{array}{l} \omega = \text{angular frequency / velocity} \\ T = \text{time period} \end{array} \right.$$

$$\omega = 2\pi f \quad \left| \quad f = \text{frequency} \right.$$


AC voltage frequency 50Hz in our country
 वायु 24 घंटा 50Hz चला (चलता चलता)

Am Sin wt
 यह Graph का
 General Equation
 $A \sin(\omega t \pm \theta)$
 ↓
 Phase

Am = Sinusoidal Graph का Amplitude
 t = (य) चला (चलता चलता) value

$\theta = 0$ এর ক্ষেত্রে Equation

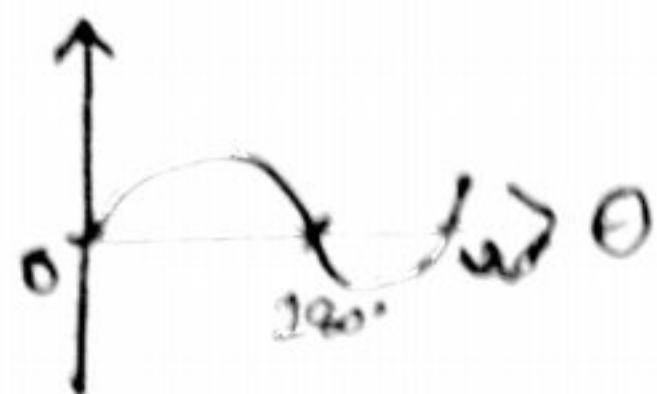Phase: \sin বা \cos ফাংশন (কোণ 270° বা 90°)




\downarrow
 $A \sin \omega t$, $\theta = 0$ (এর মূল তরঙ্গ)

$A \sin (\omega t + \theta)$ $\xrightarrow{\text{এর ক্ষেত্রে}}$ shift graph θ amount to the left.


$A \sin (\omega t - \theta)$ $\xrightarrow{\text{এর ক্ষেত্রে}}$ " " " " " right

Ex.

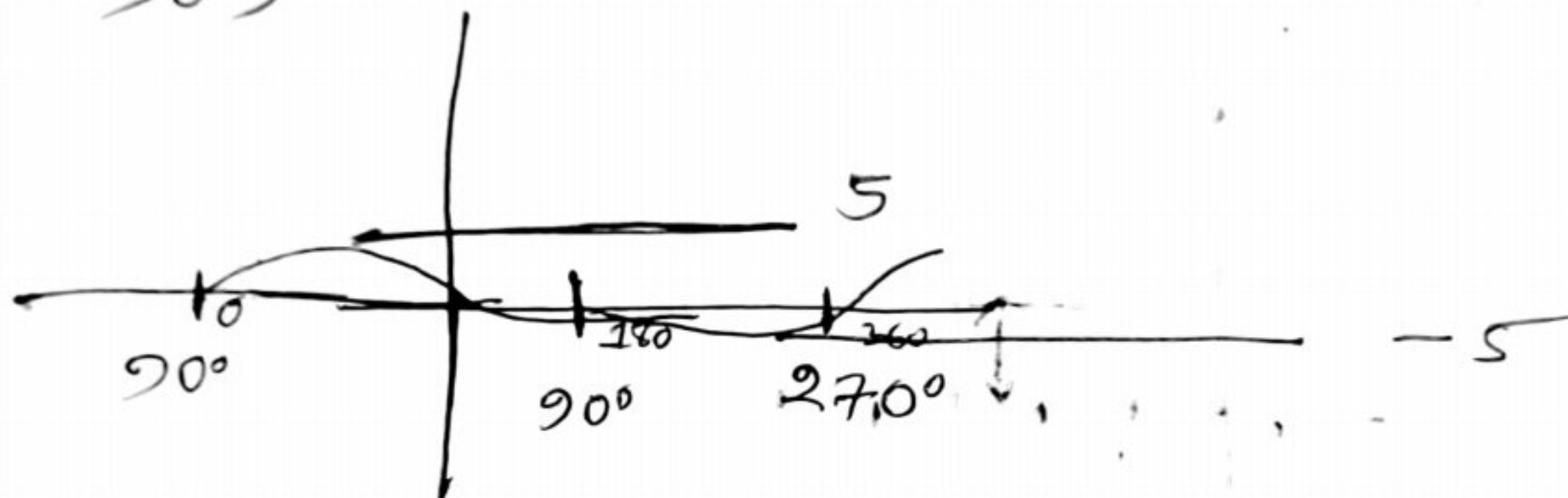$A \sin (\omega t + 90^\circ)$, যদি $A = 5$ হয়



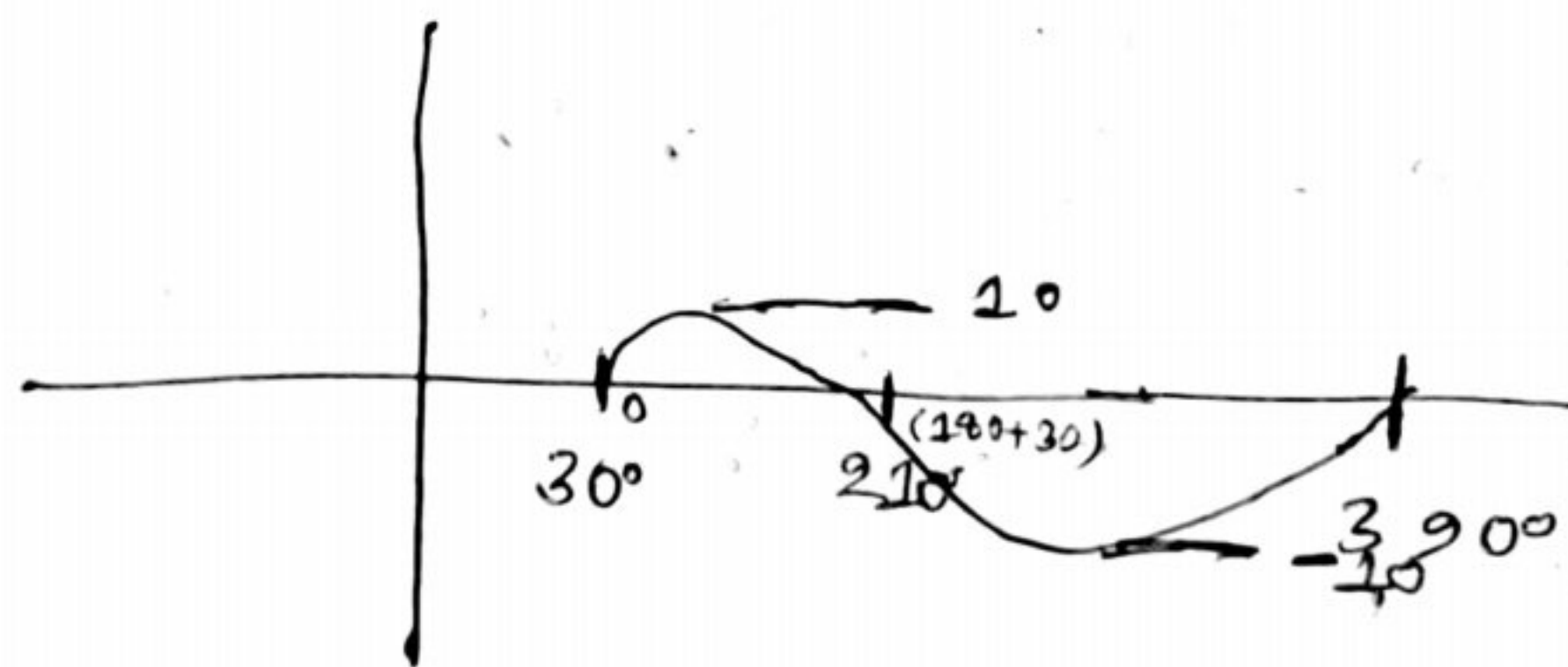$A \sin (\omega t - 30^\circ)$, যদি $A = 10$ হয়




x-13, 12

a) $V = 10 \sin (\omega t + 30^\circ)$ V

$i = 5 \sin (\omega t + 70^\circ)$ A

Sketch v & i on the same axis

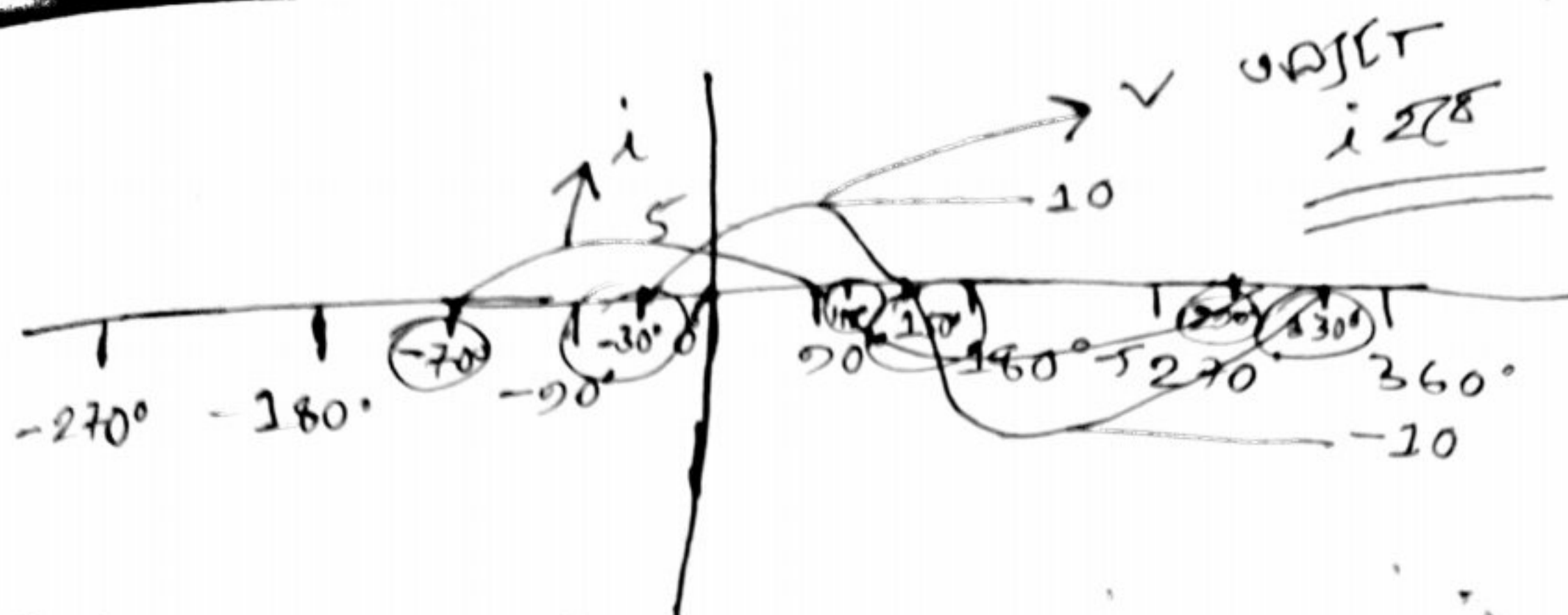

Find Phase difference between V & i
 starting point \cos -70 , -30 , 40°

$$\text{Phase difference} = | -70 - (-30) |$$

current voltage


$$= 40^\circ$$

Find the phase relationship between V & i
 Lead/Lag ; current leading by voltage

i lead V by 40°
 V lags i by 40°

$V = i \sin(2\pi \times 50 t)$, V & i are in phase

Average Value
 $V(V)$

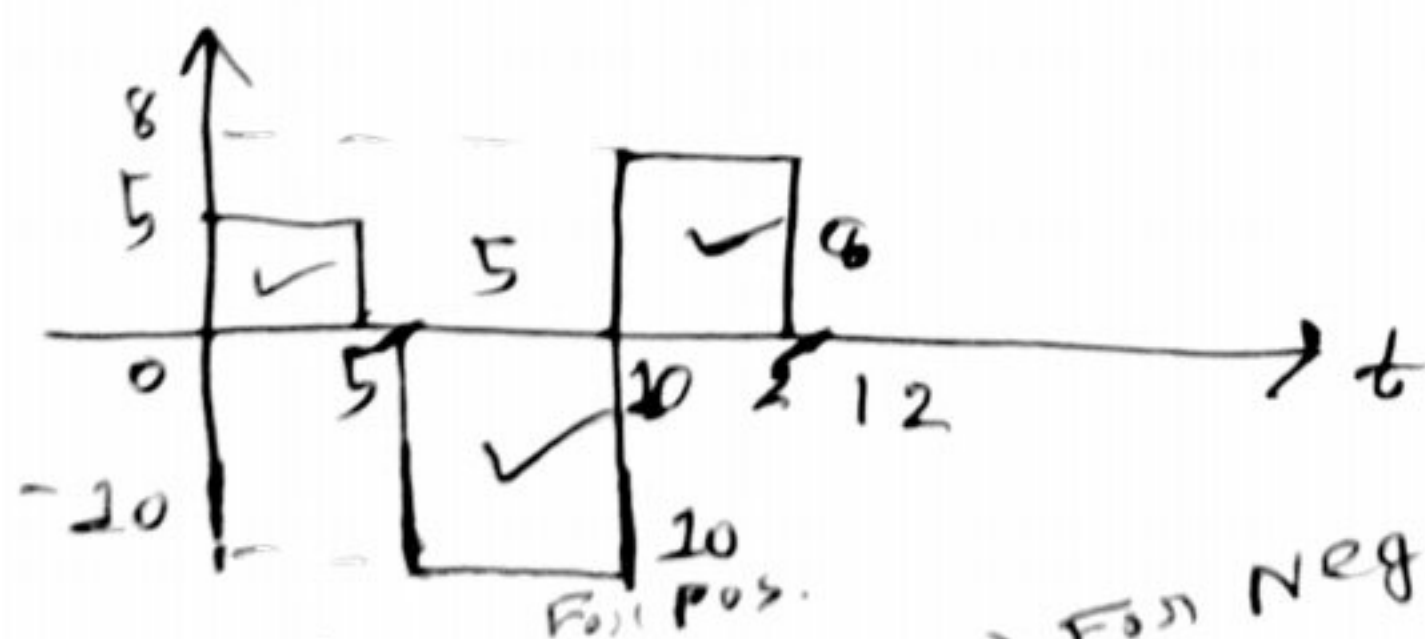

Avg Value:

$$+ (5 \times 5) - (5 \times 10) + (2 \times 8)$$


For Pos. For Neg. Area

$$\frac{\quad}{12} = -0.75 V$$

time

(y axis
is
V)

Practice:

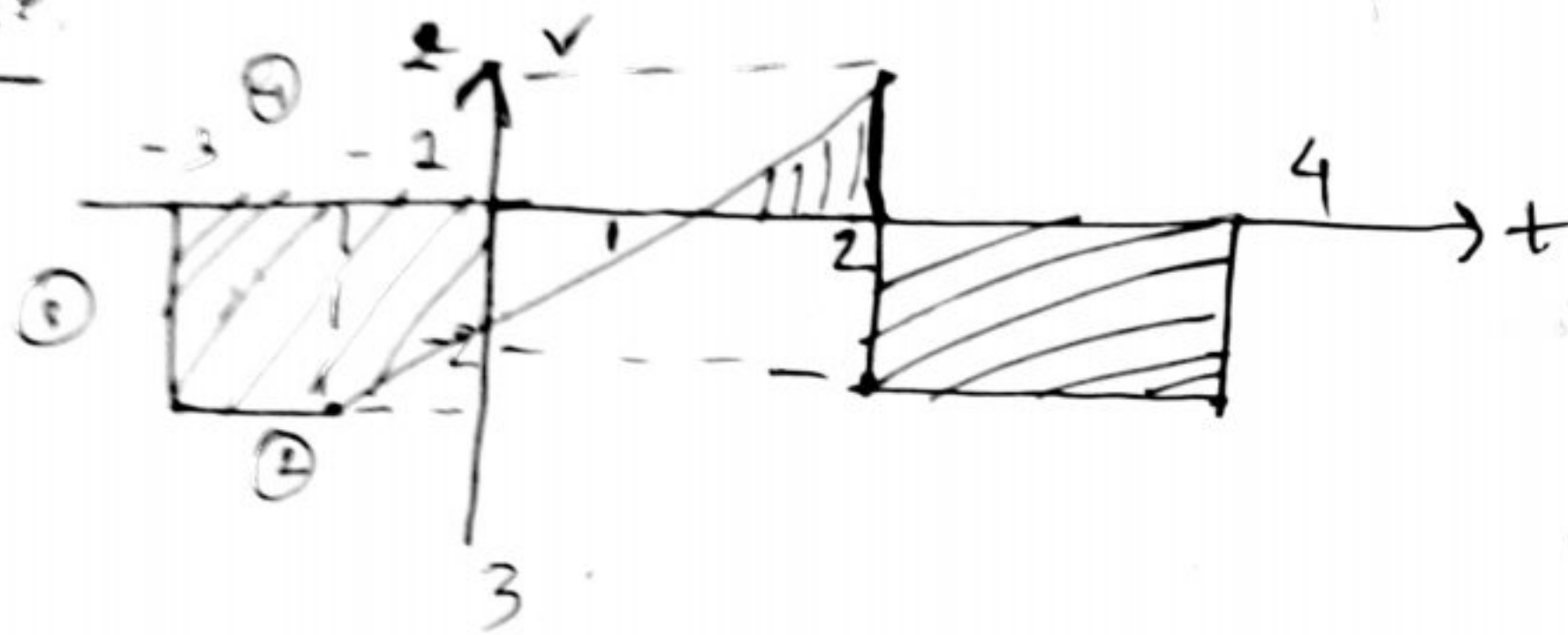


$$\text{Average} = \frac{-1/2 (4+2) \times 3 + (1/2 \times 1 \times 2) - (2 \times 2)}{7}$$

$$= -1.72$$

$$\text{Rms} = \sqrt{\frac{1/2 (4+2) \times 3^2 + (1/2 \times 1 \times 2^2) + 2 \times 2^2}{7}}$$

$$= 2.299$$

Mixed Problem:

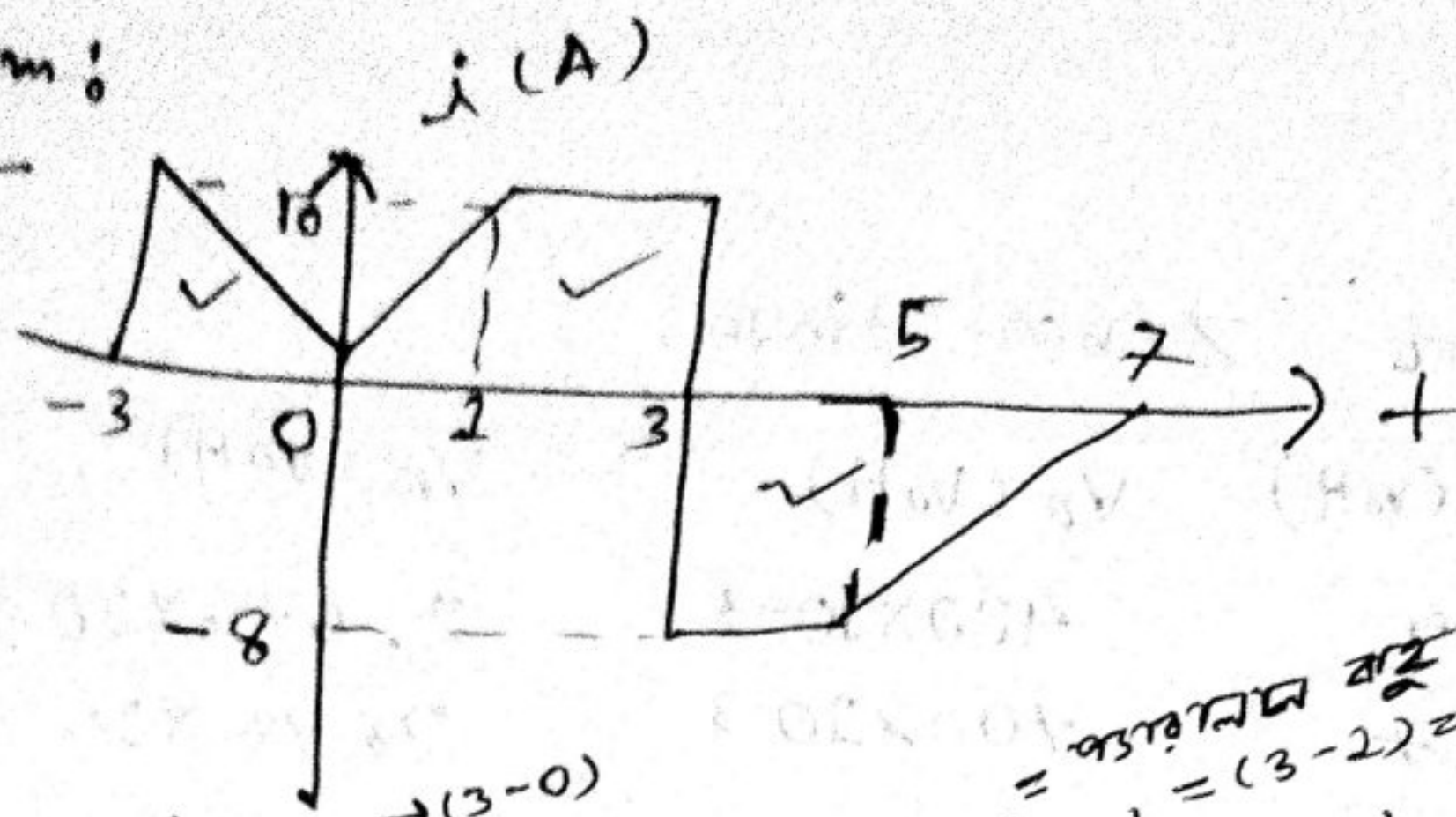

$$\text{Avg Value} = \frac{1}{2} \times 3 \times 10 + \frac{1}{2} \times (3+2) \times 10$$

[5.5] [5.5]

length = time
height = value (distance)

$$- \frac{1}{2} \times (4+2) \times 8$$

$$10 \rightarrow (7+3) = 10 = \text{distance}$$

$$= \frac{15 + 25 - 24}{10}$$

$$= 1.6 \text{ A}$$

Root Mean Square (RMS):

$$\sqrt{\frac{5 \times 5 + 5 \times 10 + 2 \times 8}{12}}$$


$$\text{RMS} = \sqrt{\frac{\frac{1}{2} \times 3 \times 10 + \frac{1}{2} \times (3+2) \times 10 + \frac{1}{2} \times (4+2) \times 8}{10}}$$

$$= 7.69 \text{ A}$$

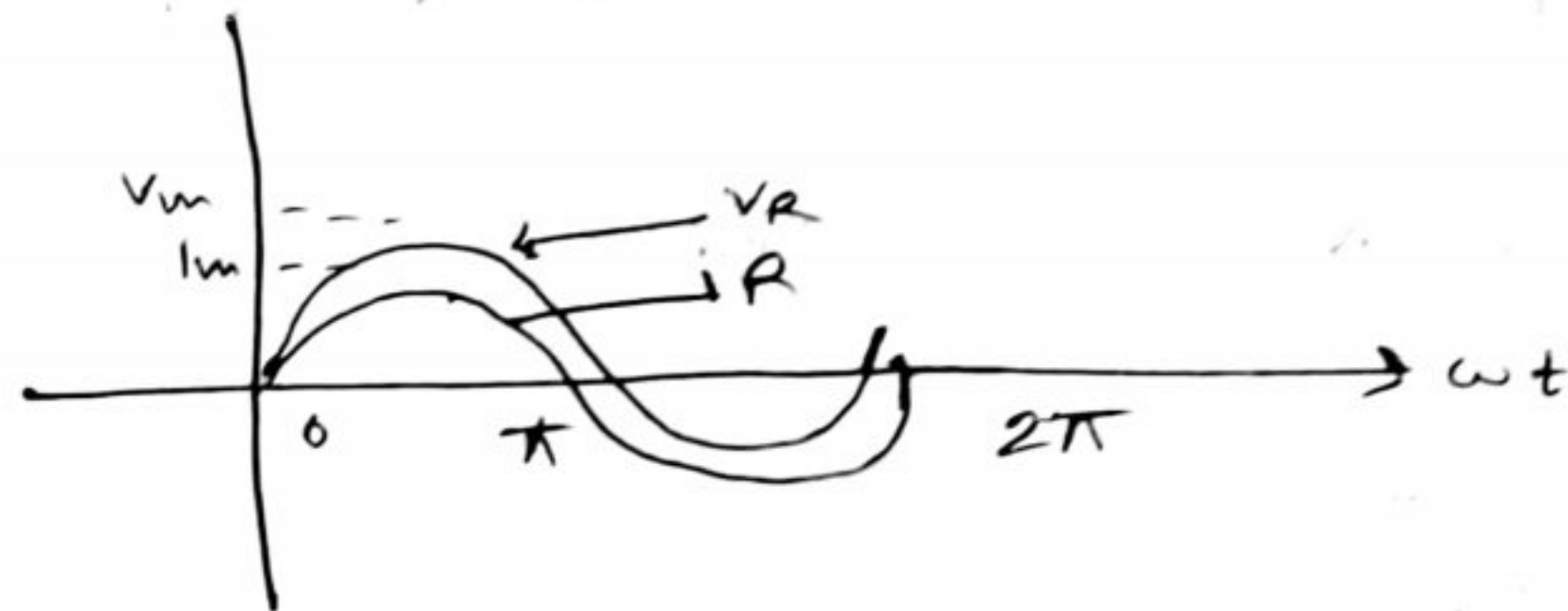
(14) The Basic Elements & Phasors

ଯଦି କେଉଁ ସାର୍ବିକ୍ ଅସ୍ତ୍ର Resistor ସାଥେ ତେବେ current ଓ voltage ସମାନ ଚାଲେ, Current ଓ voltage ଏହି ଚାଲେ (ଅଟେ) ଅସ୍ତ୍ର ଅଟେ, V and i are in phase.

$$I_m = \frac{V_m}{R} \text{ [Ohm's Law]}$$




Inductor ଏହା କ୍ଷମା [90° Fixed]

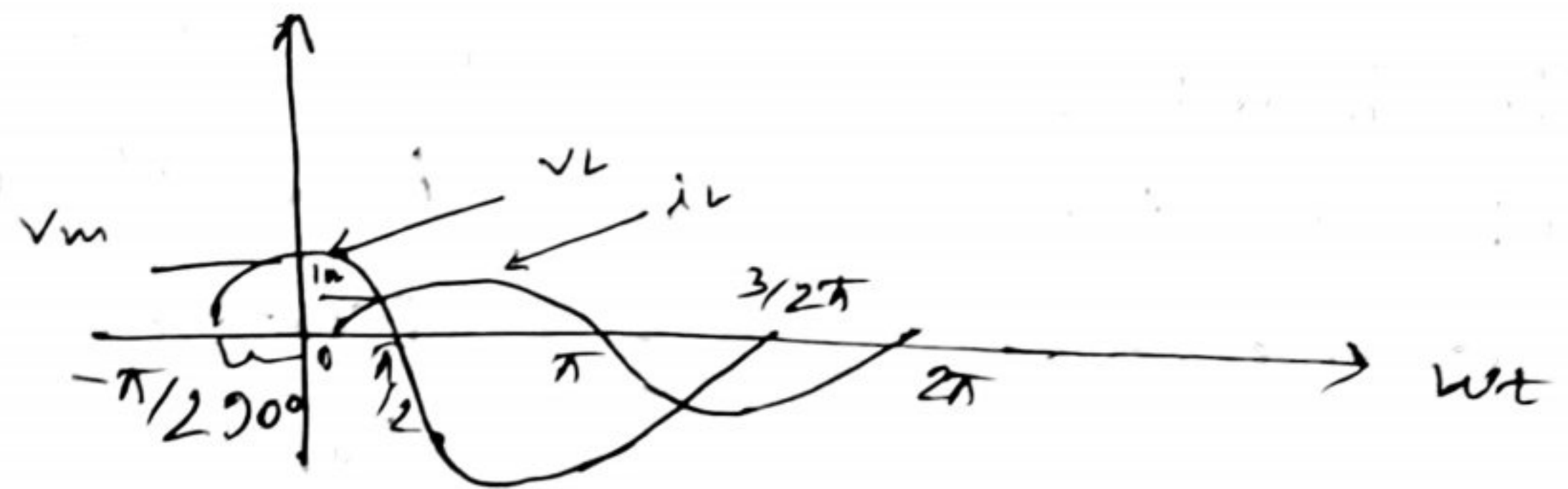

Phase difference: 90°
relationship: v leads i by 90°

Capacitor ଏହା କ୍ଷମା

i leads v by 90° → Fixed

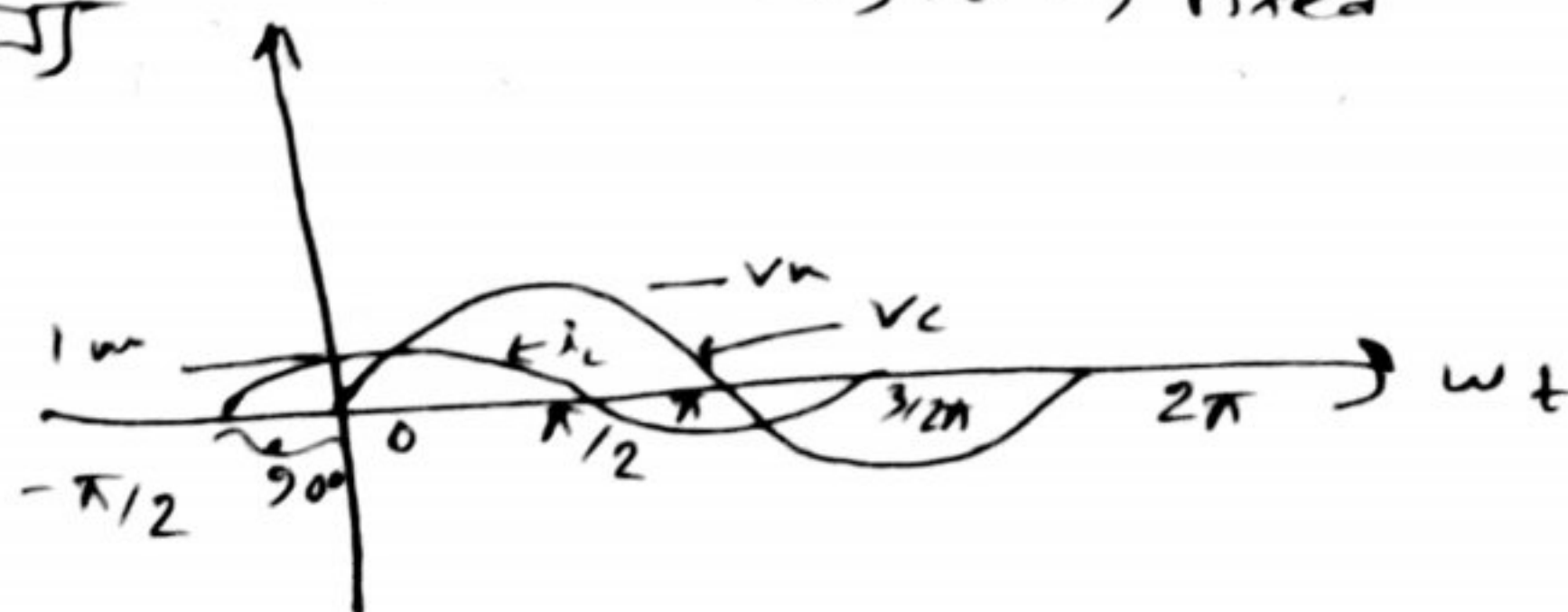

ELI the ICE
 ↓ emf
 induction voltage leads current
 ↓
 capacitor current leads voltage

for inductor: Inductive reactance $X_L = \omega L$
 " capacitor: capacitive " $X_C = \frac{V_m}{I_m}$


ω = angular velocity / frequency
 L = Inductance (H)
 f = frequency
 at 200 or 50 Hz
 or 125.27

$$X_C = \frac{1}{\omega C}$$

$$X_C = \frac{V_m}{I_m}$$

ω = angular velocity / frequency

* DC source or frequency

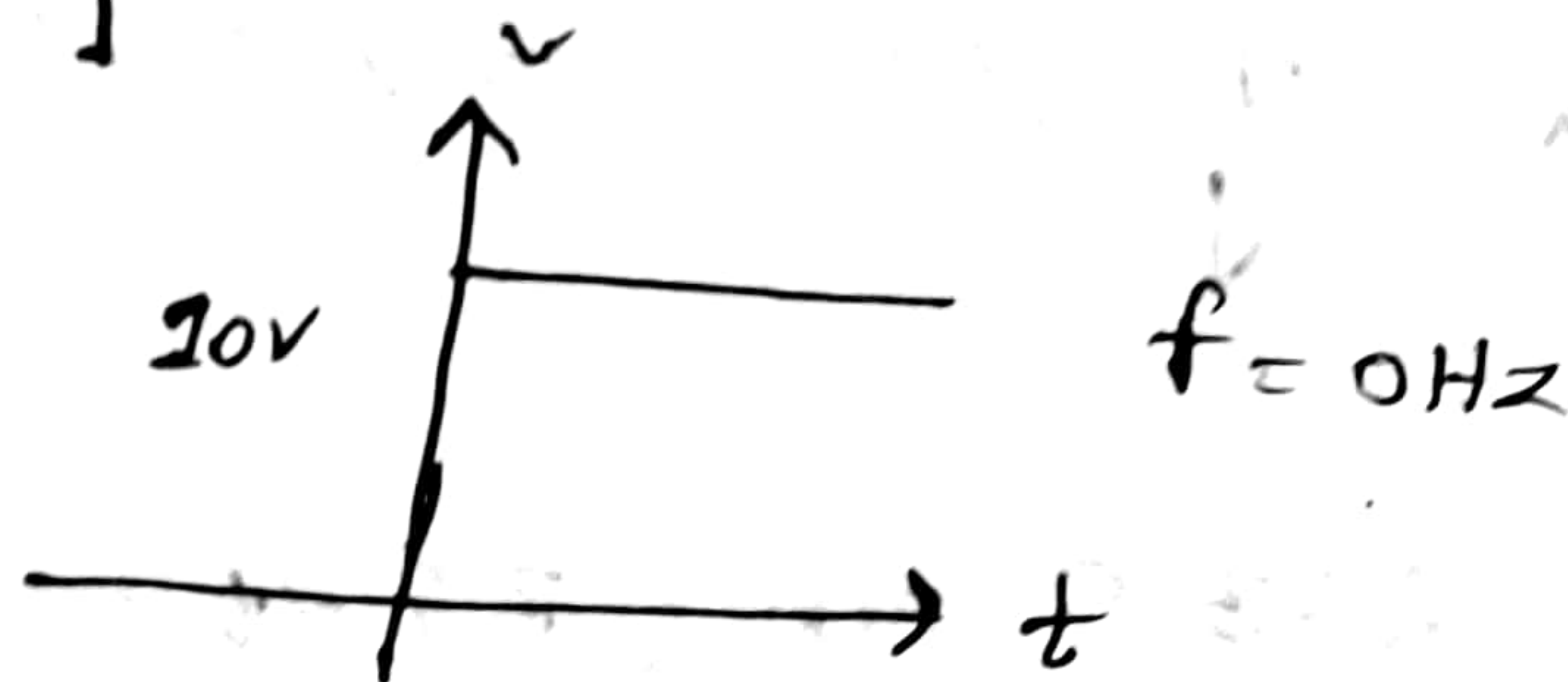

$\therefore X_L = 2\pi \times 0 \times L = 0 \Omega$ [short circuit or Resistance 0]
 $X_C = \frac{1}{2\pi \times 0 \times C} = \infty$ [open " " " "]

Ex 14.1

b) $v = 25 \sin(377t + 60^\circ)$, across resistor


$$R = 10 \Omega$$

$$I_m = \frac{V_m}{R} = \frac{25}{10} = 2.5 \text{ A}$$

$m = \text{maximum}$

Resistor or (resistor) current 3 voltage or (voltage) or (current) or (voltage) or (current)

$$i = 2.5 \sin(377t + 60^\circ)$$

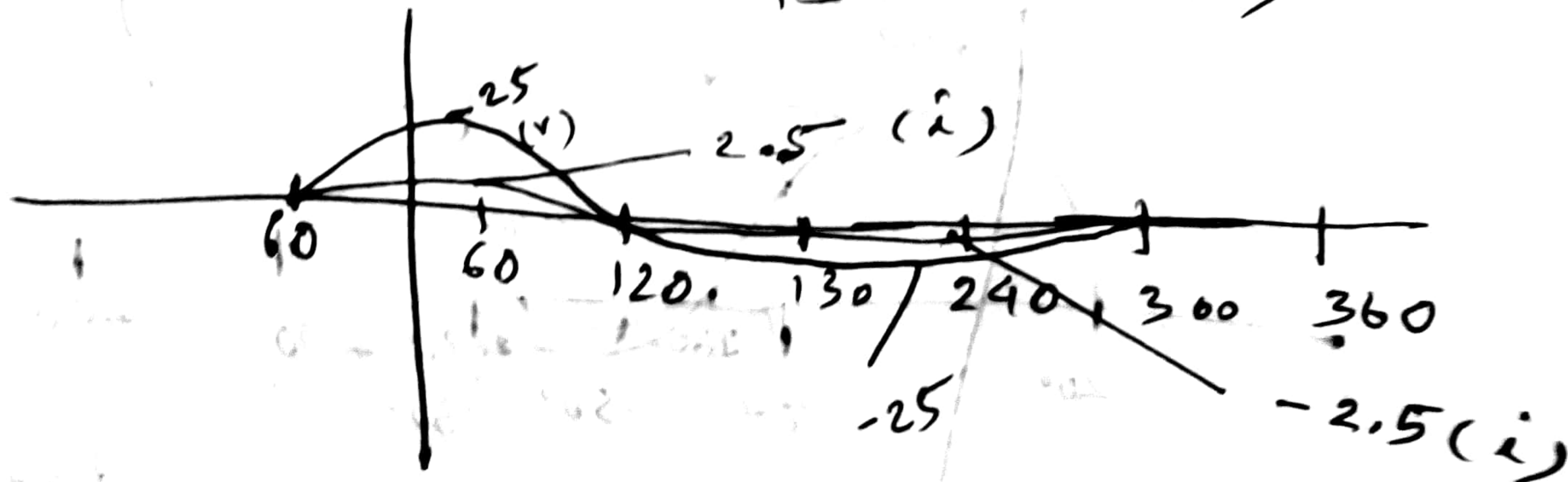

Ex - 14.3

b) $L = 0.1 \text{ H}$

$$i = 7 \sin(377t - 70^\circ) \text{ A}$$

$$A \sin(\omega t - \theta)$$

Sketch v on the same axis

$$V_m = I_m \times X_L \left[\because X_L = \frac{V_m}{I_m} \right]$$


$$X_L = \omega L = 2\pi fL$$

$$= 377 \times 0.1 = 37.7 \Omega$$

$$V_m = \underset{\substack{\downarrow \\ \text{A}}}{I_m} \times L = 7 \times 37.7 = 263.9 \text{ V}$$

$$V = 263.9 \sin(377t - 70^\circ + 90^\circ)$$

current -70° (right shift)


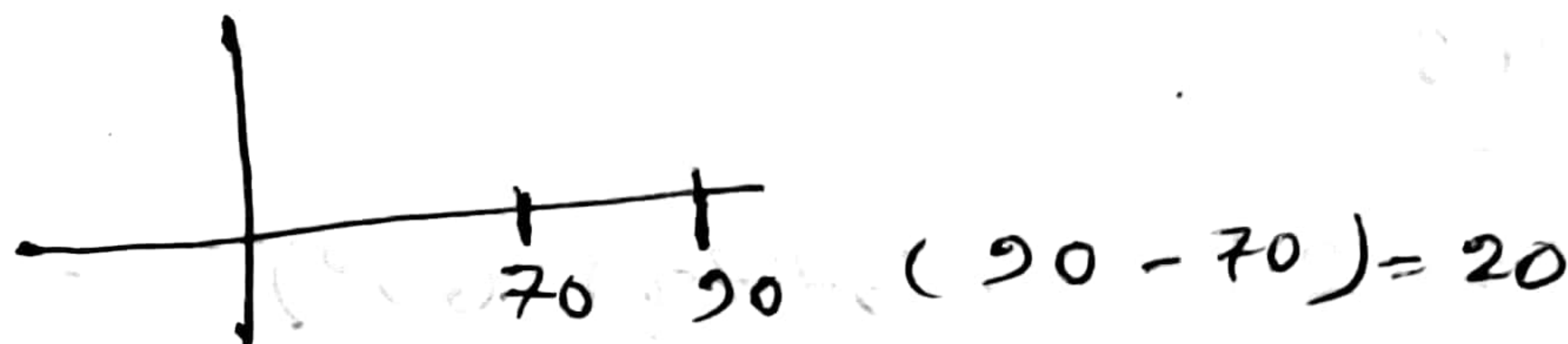


Example

$$v = 50 \sin(377t + 50^\circ)$$

$$i = 5 \sin(377t + 50^\circ - 90^\circ)$$

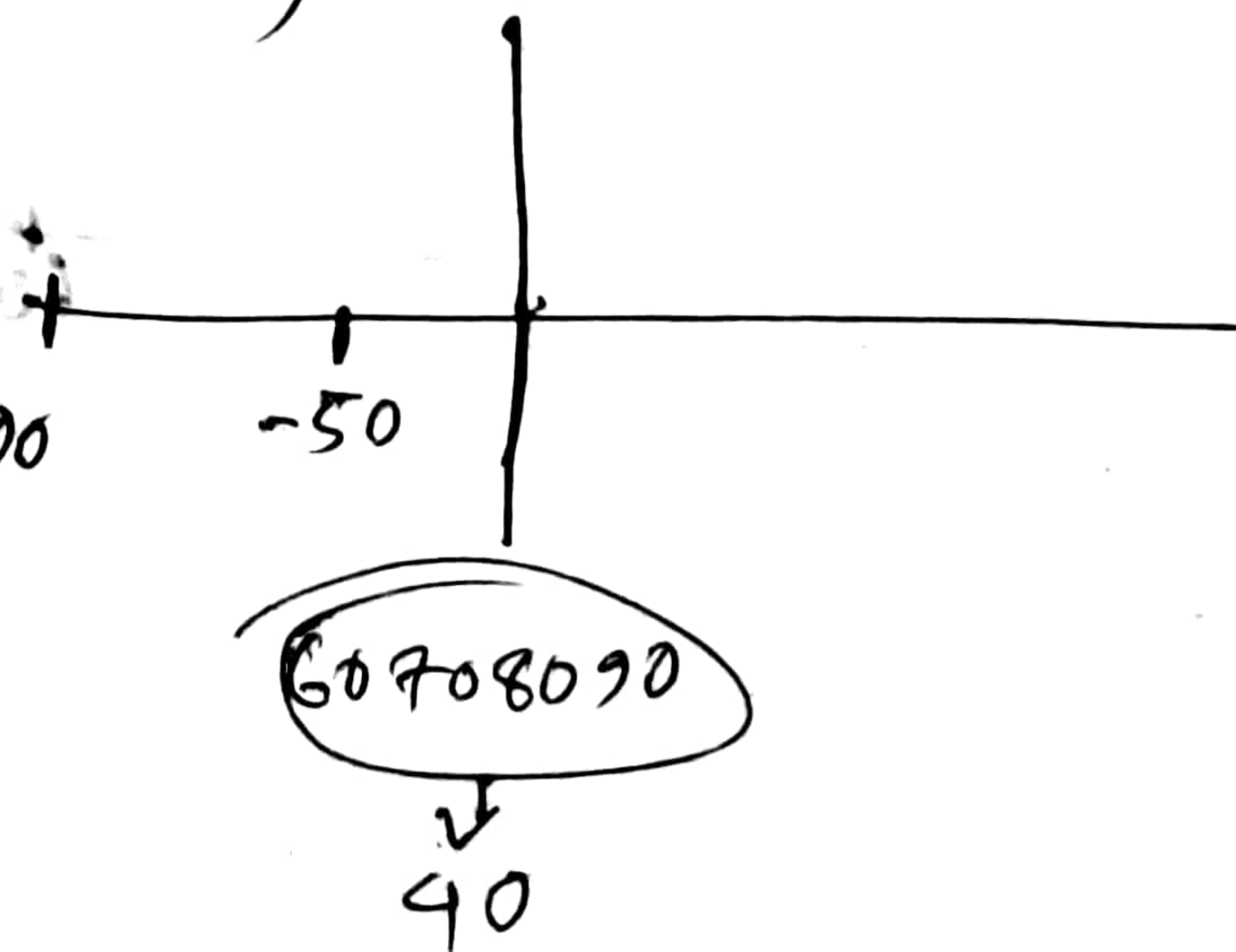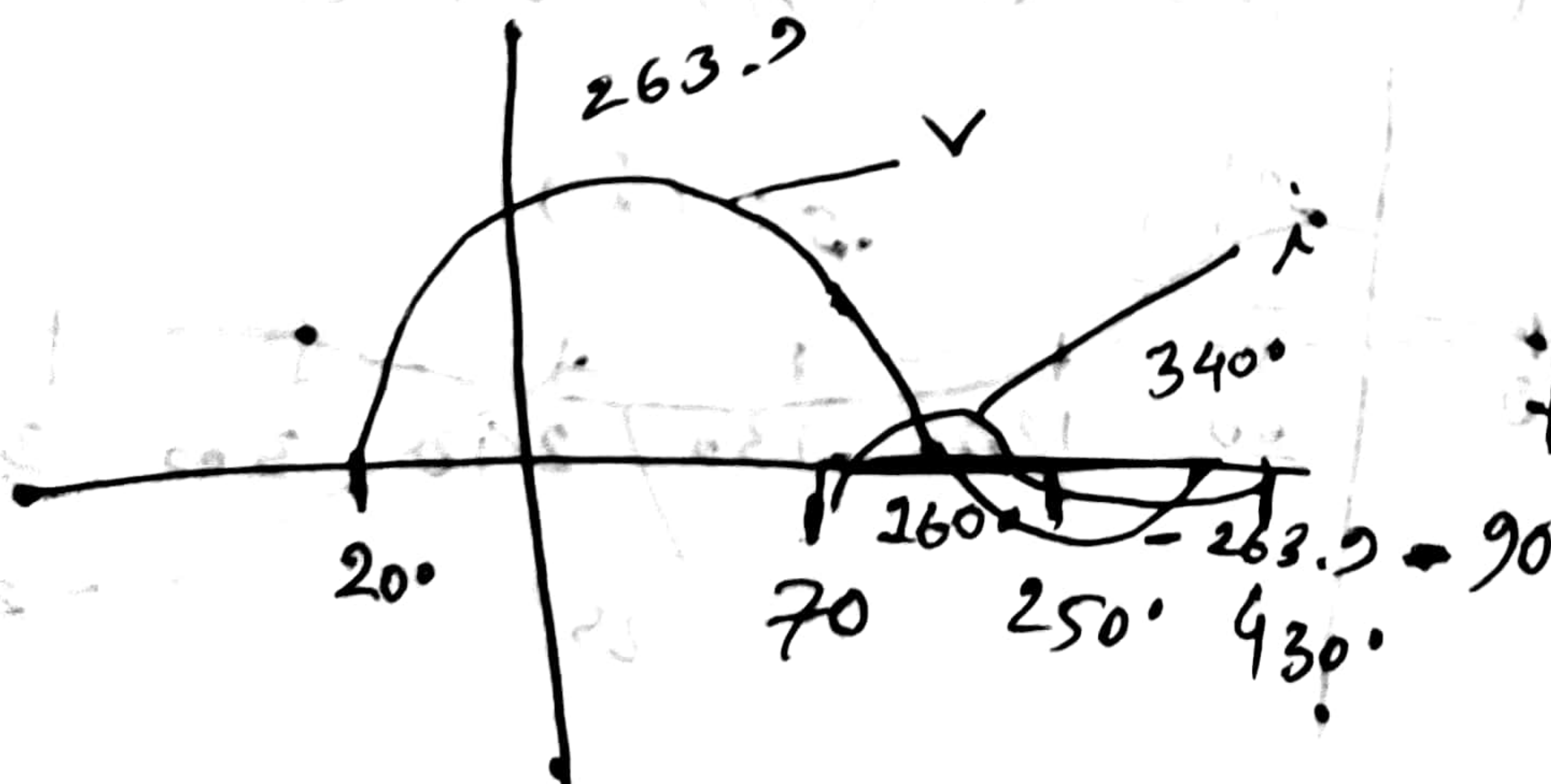
inductor \therefore Voltage leads current



Ex-24.4 (inductor)
 Ex-24.5 (capacitor)

$$C = 100 \mu F$$

$$i = 40 \sin(500t + 60^\circ)$$

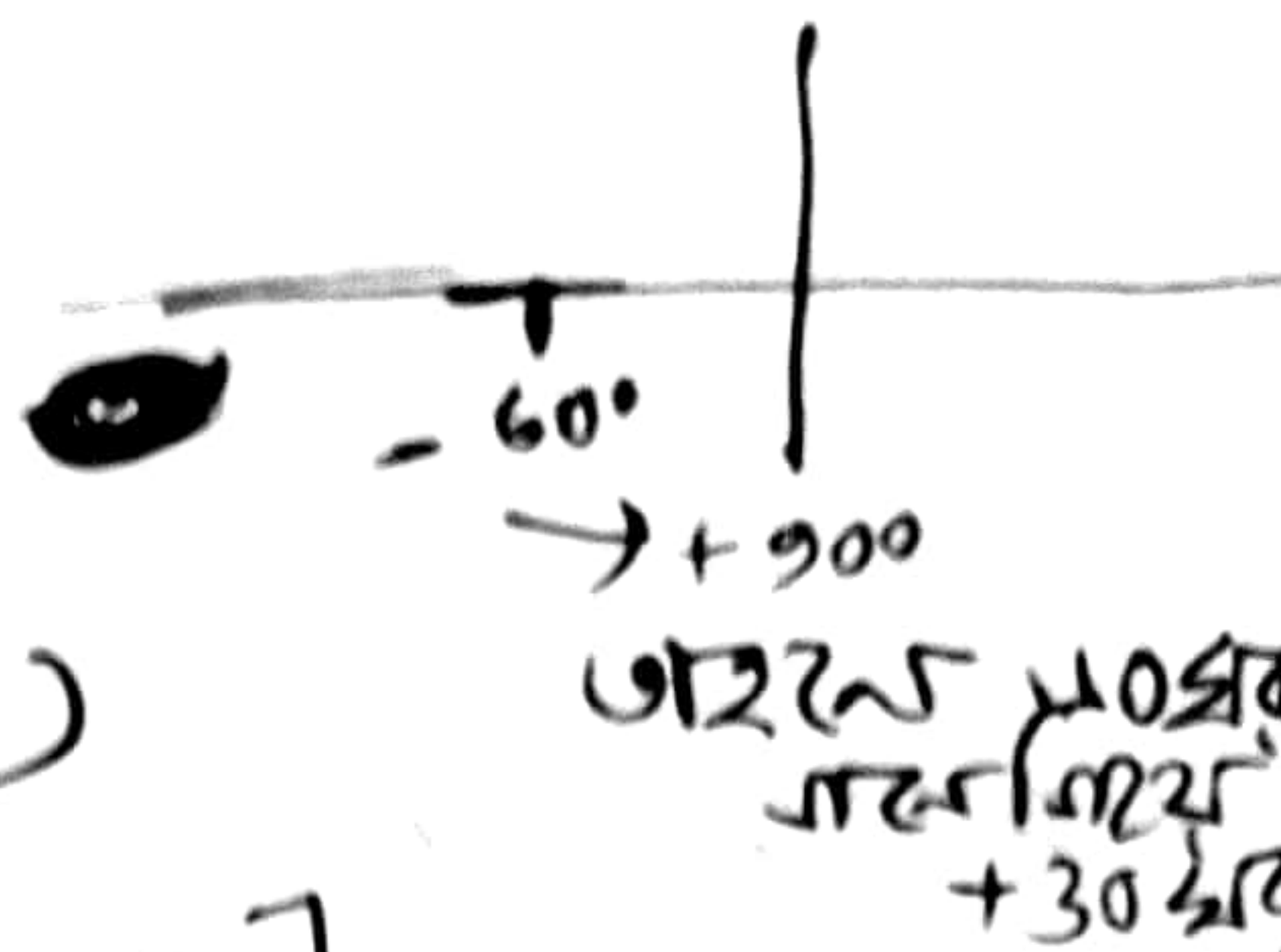

$I \angle E$
 current leads voltage


$$I_m = 40 A$$

$$\rightarrow [v = iR]$$

$$V_m = I_m X_C = 40 \times 20 = 800$$

$$X_C = \frac{1}{\omega C} = \frac{1}{500 \times 100 \times 10^{-6}} = 20 \Omega$$

$$v = 800 \sin(500t - 30^\circ)$$

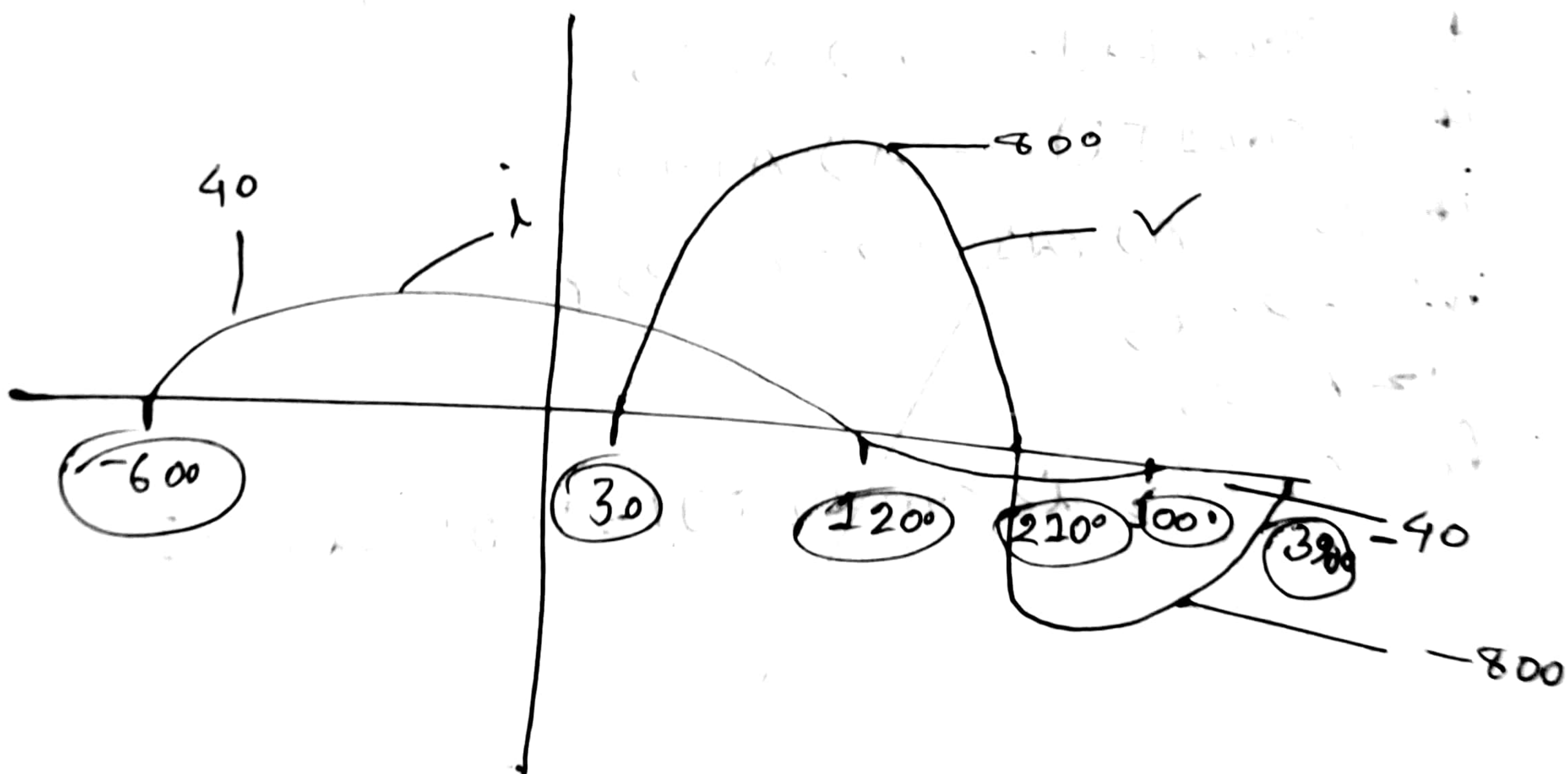

$$\frac{0^\circ + 30}{180^\circ + 30}$$

$$\frac{360^\circ + 30}{360^\circ + 30}$$